

Department of Computer Science and Engineering, Dhaka University
First In-Course Examination
1st Year 1st Semester, Session: 2015-2016
EEE – 1103, Electrical Circuits

Total Marks: 35

Time: 1 Hour

1. a) Define power and energy. 3
 b) i) Given no load voltage 120 V and full load voltage 118 V with full load current 10 A, 4
 determine the voltage regulation of the supply.
 ii) Determine the internal resistance of the supply.
2. a) Read the following information regarding the series circuit and write down the counterpart/
 complementary statement for the parallel circuit. 4
 i) *The total resistance of a series configuration is the sum of the resistance levels.*
 ii) *The more resistors we add in series, the greater the resistance, no matter what their
 value.*
 iii) *The largest resistor in a series combination will have the most impact on the total
 resistance.*
 iv) *The current is the same at every point in a series circuit.*
- b) Using Kirchhoff's voltage law, find the unknown voltages for the configurations in **Fig. 1**. 3

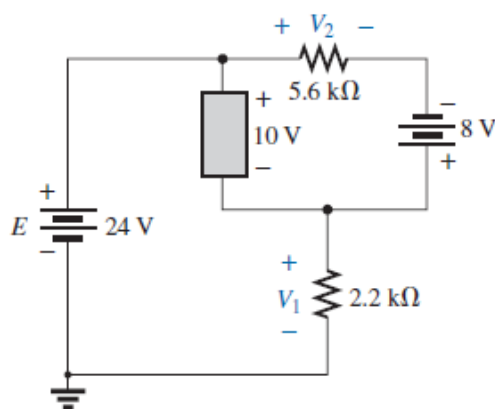


Fig.1

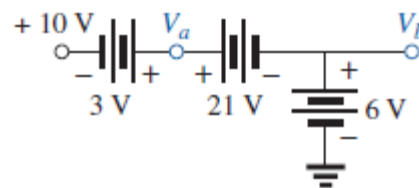


Fig 2

- c) Determine the voltages V_a , V_b , and V_{ab} for the networks in **Fig. 2**. 3
- d) For the integrated circuit in **Fig. 3**, determine V_0 , V_{03} , V_2 , V_{23} , V_{12} , and I_i . 4

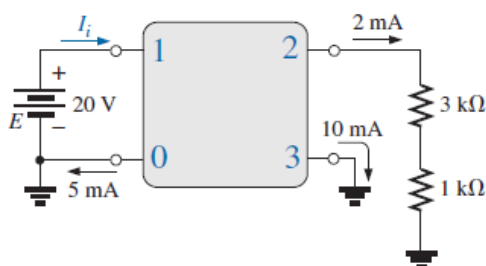


Fig. 3

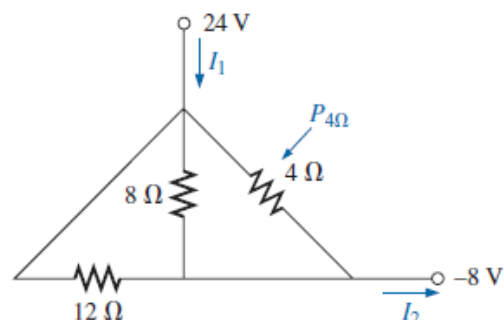


Fig. 4

3. a) Find the unknown quantities for the networks in **Fig. 4** using the information provided. 4
 b) Using Kirchhoff's current law, determine the unknown currents for the networks in **Fig. 5**. 3
 c) Assuming identical supplies, determine the current I and resistance R for the parallel
 network in **Fig. 6**. 4
 d) Determine the voltage V and the current I for the network in **Fig. 7**. 3

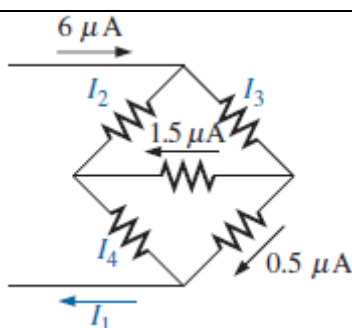


Fig 5

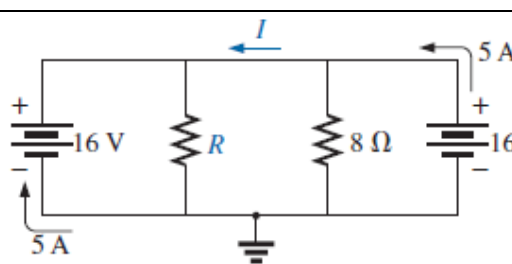


Fig. 6

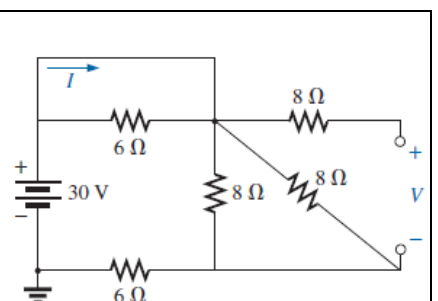


Fig. 7