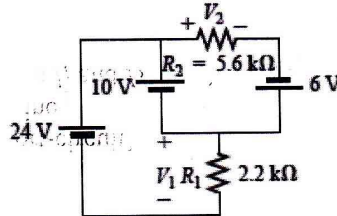



Total Marks: 35

Time: 1 Hour


1. a) State Kirchhoff's voltage law with a suitable figure. 3
- b) Determine the unknown voltages using Kirchhoff's voltage law. 3



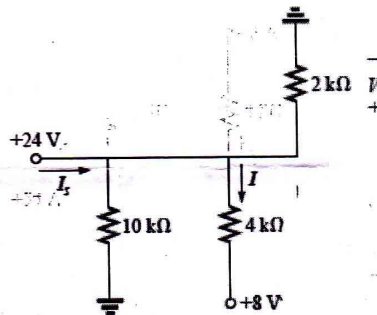- c) The no-load and full-load voltages of a power supply are 120 V and 100 V respectively. Calculate the voltage regulation of the power supply. 2
2. a) "For parallel resistors, the total resistance will always increase as additional elements are added in parallel". Do you agree? Give proof in favor of your opinion. 4
- b) For the network below 5
 - i) Find the current I
 - ii) Determine the voltage V
 - iii) Calculate the source current I_s



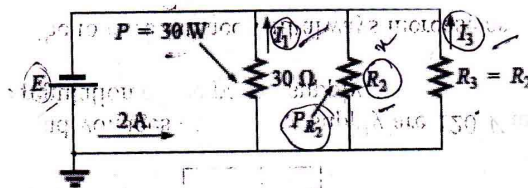3. a) What are the rules for dividing current in a parallel circuit? Also find the generic equation. 4
- b) Find the unknown quantities for the circuit using the information provided. 5



4. a) Define 'Open-circuit' and 'Short-circuit'. 4
- b) For the network below, determine 5
 - i) The short-circuit currents I_1 and I_2
 - ii) The voltages V_1 and V_2
 - iii) The source current I_s

